

Fig. 1. Circuit diagram of the complete power supply 20 volt 2.5 ampere version.

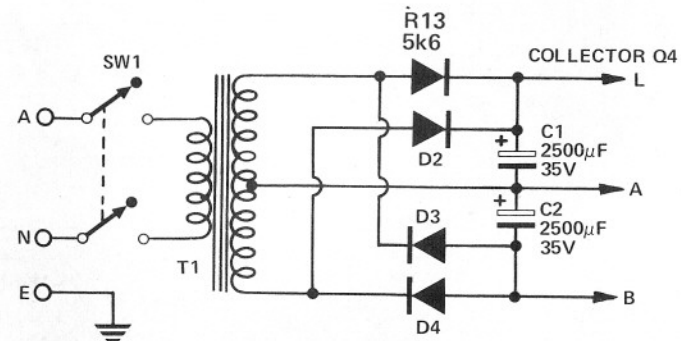


Fig. 2. Alternative rectifier and filter capacitor connections required for 40 volt, 1.25 ampere version.

RECONNECTED POWER SUPPLY FOR 40V 1.25A SUPPLY